

Objective

After finishing this training, you will be able to

- Understand the history of VHDL

- Understand the synthesis process

- Become familiar with structure and syntax

- Implement combinatorial and registered components with the language

- Complete a VHDL design in ISP Lever System

Introduction

VHSIC Hardware Description Language

VHSIC - Very High Speed Integrated Circuit

Intended by DoD as a standard means to document complex circuit among contractors

Established as IEEE standard 1076 in 1987

Updated as IEEE standard 1164 in 1993

Nowadays VHDL is used to

- Document circuits

- Synthesize design descriptions

- Simulate circuits

About VHDL

Advantages

Device-independent design

do not have to be familiar with device architectures

Portability

same description for synthesis and simulation tools

same description for different platforms

Fast time-to-market and low cost

facilitates speedy design process and design iteration


Possible Shortcomings

Loss control of defining gate-level circuit implementation

Inefficient logic implementations created by synthesis tools

About Synthesis

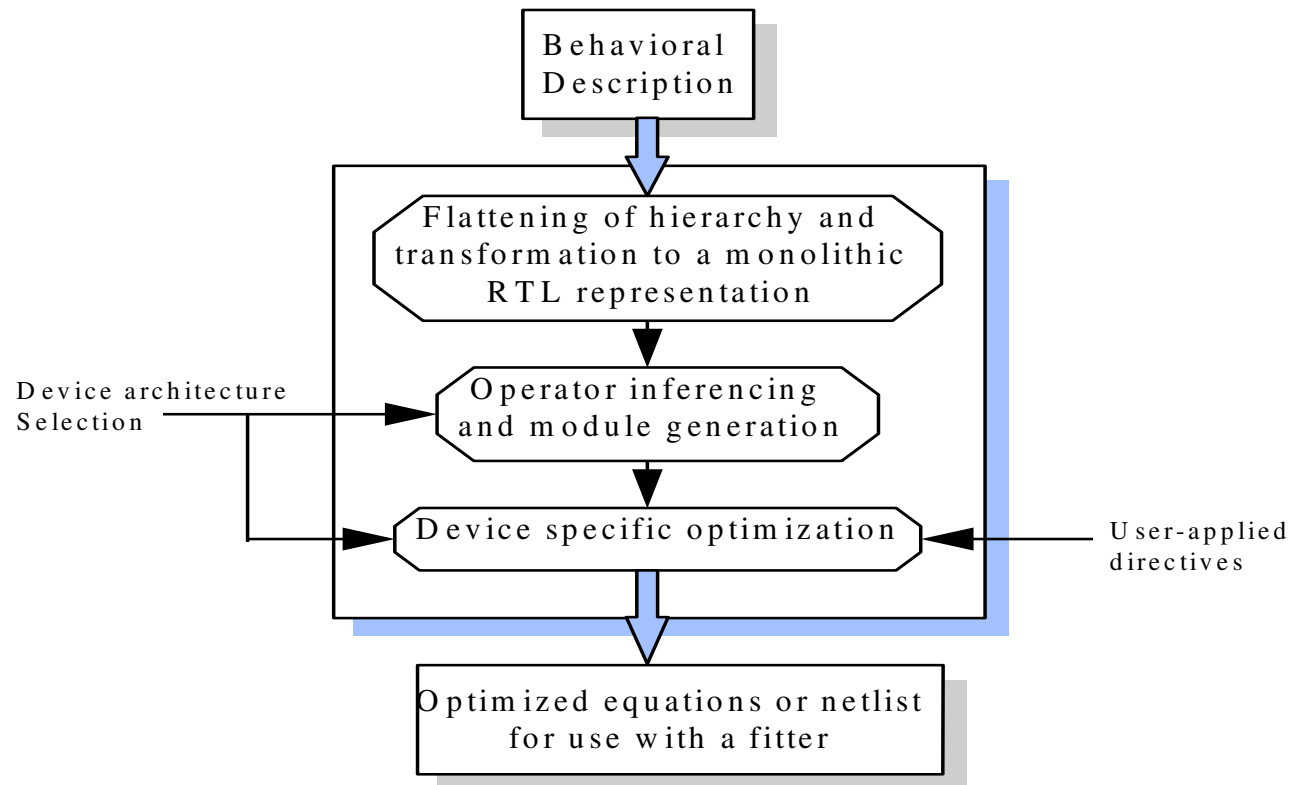
It is the realization of design descriptions into circuits
VHDL synthesis tools convert VHDL descriptions to technology-specific equations and netlists



VHDL Design Descriptions

VHDL design descriptions consist of an ENTITY and ARCHITECTURE pair

The ENTITY describes the design I/Os

 

The ARCHITECTURE describes the content of the design

Structural Description:

- Instantiation of building blocks referred to as components

- Schematic type of placement and connections

Behavioral Description:

- Abstract descriptions and Boolean equations

- Increase productivity, portability and readability of the design

VHDL Overview



Bringing the Best Together

```
LIBRARY ...;
USE ...;
ENTITY black_box IS
    PORT    ( ... );
END black_box;
```

Libraries

Entity

Port

```
ARCHITECTURE black_box_arch OF black_box IS
    -- global signal declarations
    -- global constant declarations
```

Architecture
Declarations

```
BEGIN
    name:PROCESS(sensitivity list)
        -- local variable declarations
    BEGIN
        -- sequential statements
    END PROCESS name;
```

Processes

...

```
-- concurrent statements
```


...

```
END black_box_arch;
```

Concurrent
statements

The Entity - example

VHDL description of the black box:

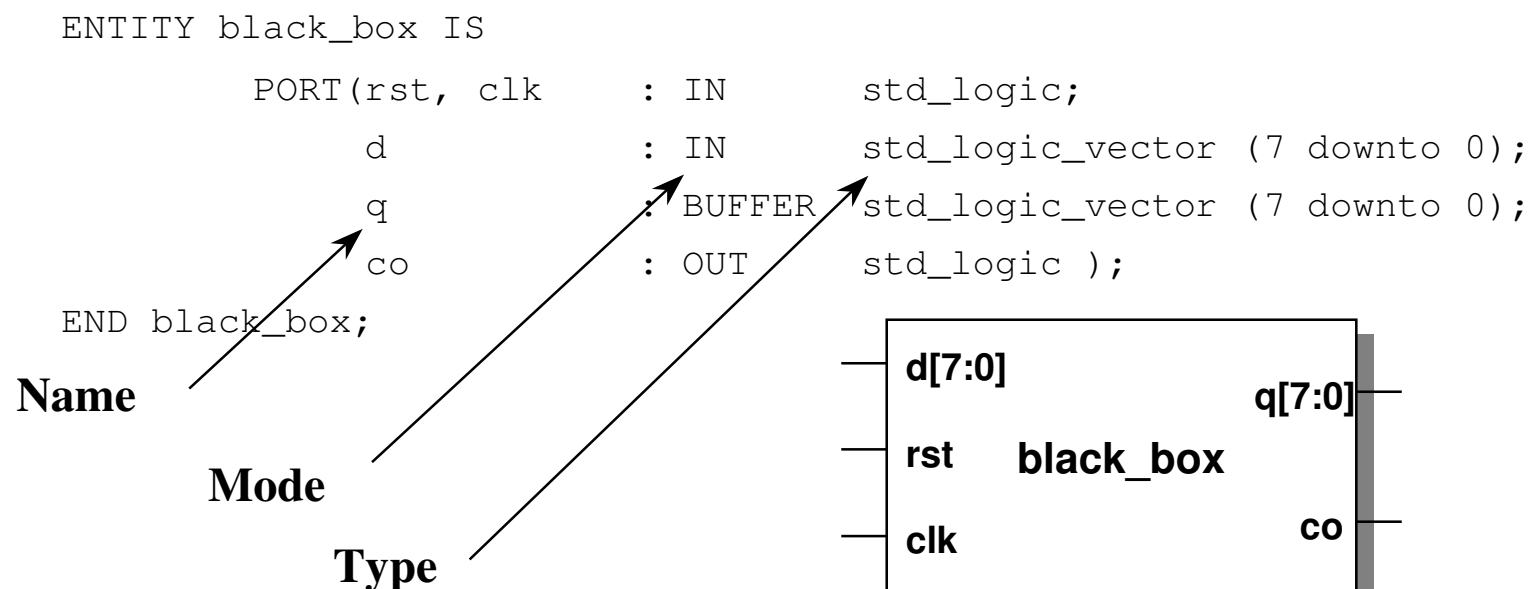

Names can be chosen by designer, BUT no reserved words,
no äöüß..., no number as first character

VHDL Reserved Words

Use of reserved words as names will cause errors

ABS	ELSE	NAND	SELECT
ACCESS	ELSIF	NEW	SIGNAL
AFTER	END	NEXT	SUBTYPE
ALIAS	ENTITY	NOR	
ALL	EXIT	NOT	THEN
AND		NULL	TO
ARCHITECTURE	FILE		TRANSPORT
ARRAY	FOR	OF	TYPE
ATTRIBUTE	FUNCTION	ON	
		OPEN	UNITS
BEGIN	GENERIC	OR	UNTIL
BLOCK		OTHERS	USE
BODY	IF	OUT	
BUFFER	IN		VARIABLE
BUS	INOUT	PACKAGE	
	IS	PORT	WAIT
CASE		PROCECURE	WHEN
COMPONENT	LABEL	PROCESS	WHILE
CONSTANT	LIBRARY		WITH
	LINKAGE	RANGE	
DOWNTO	LOOP	RECORD	XOR
		REGISTER	XNOR
	MAP	REM	
		REPORT	
		RETURN	

The Entity

Points of communication of ENTITY are PORTs

Always associate with I/Os of a components or device pins

Similar to “symbols” in a schematic

Does not describe the function of the block

Each PORT must have

A name: must be unique within ENTITY

A list of properties

a direction - known as MODE

a value the PORT can take - known as TYPE

PORT Modes

IN	A signal that goes into the entity but not out
OUT	A signal that goes out of the entity but not in and is <u>not used internally</u>
INOUT	A signal that is bidirectional (goes into and out of the entity)
BUFFER	A signal that goes out of the entity and is also fed-back internally within the entity
BUFFER	is a subset of INOUT but it is not driven externally

PORT Types

VHDL is a strongly typed language. You cannot assign one signal type to another signal type

`integer` Useful as index holders for loops and constants.
Not usually used for I/O signals.

`boolean` Can take values of 'TRUE' and 'FALSE'

**control
structures**

`std_logic` Standard industry logic type, has values of '0', '1', 'X',
and 'Z' defined by IEEE std 1164.

`std_logic_vector` A grouping of `std_logic`, standard
industry logic type, definition for busses

**hardware
signals**

The ENTITY - Example

`d` is a 16-bit input bus


`clk`, `reset` and `oe` are input signals

`q` is a 16-bit tri-stateable output bus

`ad` is a 16-bit bi-directional bus

`int` is an output signal, that is also sensed internally

`as` is a tri-stateable output signal

 

The Entity - Example

```
ENTITY my_design1 IS
    PORT (d          : IN          std_logic_vector (15 downto 0);
          clk,reset,oe : IN          std_logic;
          q          : OUT          std_logic_vector (15 downto 0);
          ad         : INOUT       std_logic_vector (15 downto 0);
          int        : BUFFER      std_logic;
          as         : OUT          std_logic );
END my_design1;

--          q : OUT std_logic_vector (15 downto 0);
--          MSB = q(15) ; LSB = q(0);
--          q : OUT std_logic_vector (0 to 15);
--          MSB = q(0) ; LSB = q(15);

-- Two dashes indicate a comment line in VHDL
```

The Architecture



Bringing the Best Together

```
ARCHITECTURE black_box_arch OF black_box IS
```

```
    -- global signal declarations  
    -- global constant declarations
```

```
BEGIN
```

```
    name:PROCESS(sensitivity list)  
        -- local variable declarations  
    BEGIN  
        -- sequential statements  
    END PROCESS name;
```

```
    ...
```

```
    -- concurrent statements
```

```
    ...
```

```
END black_box_arch;
```

Architecture
Declarations

Processes

Concurrent
statements

The Architecture

ARCHITECTURE describes what is in the ENTITY

It describes the behavior of the design

ARCHITECTURE contains the following statements:

Concurrent statements and PROCESS statements:

Statements outside of a PROCESS statement are “concurrent statements”.

These statements and processes are evaluated concurrently and are evaluated independently of the order in which they appear.

Sequential statements :

Statements within a PROCESS statement are “sequential statements” and are evaluated sequentially in terms of simulation.

The Architecture - example

```
-- This example is simple logic

ENTITY logic IS
    PORT (a,b      : IN   std_logic;
          w, x, y  : OUT  std_logic;
          z        : OUT  std_logic_vector (3 downto 0) );
END logic;

ARCHITECTURE behavior OF logic IS

BEGIN

    y <= (a AND b);
    w <= (a OR b);
    x <= '1';
    z <= "0101";

END behavior;
```


Libraries

Library is a place to keep *precompiled packages* so that they can be used in other designs

```
LIBRARY ieee; -- symbolic name for IEEE standard library
USE ieee.std_logic_1164.ALL; -- name of the package
USE ieee.std_logic_unsigned.ALL;
```

The “ieee.std_logic_unsigned” library allows the use of certain operators on “std_logic” type signals.

eg. `(count <= count + 1;)`

Do not mix signed and unsigned!!! (scope of USE is file)

Entity / Architecture / Libraries - example



Every design has an ENTITY/ARCHITECTURE pair

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY logic IS
    PORT (
        a,b      : IN    std_logic;
        w, x, y   : OUT   std_logic;
        z         : OUT   std_logic_vector (3 downto 0) );
END logic;

ARCHITECTURE behavior OF logic IS
    BEGIN

        y <= (a AND b);
        w <= (a OR b);
        x <= '1';
        z <= "0101";
    END behavior;
```

Concurrent Statements - examples

Concurrent statements include

boolean equations

```
x <= (a AND (NOT sel1)) OR (b AND sel1);  
g(0) <= NOT (y AND sel2);
```

conditional assignments (i.e., when...else...)

```
y <= d WHEN (sel1 = '1') ELSE c;  
g(1) <= '0' WHEN (x = '1' AND sel2 = '0') ELSE '1';  
z <= "01010101"; -- Binary assignment  
z <= x"55"; -- Hexadecimal assignment
```

instantiations

```
inst1: fd11 PORT MAP (d=>din, clk=>clka, q=>qout);
```

WITH - SELECT - WHEN

Used for concurrent signal assignment (Example):

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY mux IS
    PORT (a, b, c, d : IN    std_logic;
          s           : IN    std_logic_vector(1 downto 0);
          x           : OUT   std_logic );
END mux;

ARCHITECTURE mux_with OF mux IS
BEGIN
    WITH s SELECT
        x <= a WHEN "00",    -- x is assigned based on s
           b WHEN "01",
           c WHEN "10",
           d WHEN "11";
END mux_with;
```

WHEN - ELSE

Same example of 4-to-1 mux

```
ARCHITECTURE mux_when OF mux IS
BEGIN
    x <= a WHEN ( s = "00" ) ELSE
        b WHEN ( s = "01" ) ELSE
        c WHEN ( s = "10" ) ELSE
        d;
END mux_when;
```

WITH-SELECT-WHEN must specify mutually exclusive conditions

WHEN-ELSE does not have to

Standard VHDL Operators

Logical Operators

AND
OR
XOR
NOT

Relational Operators

=	Equal to
/=	Not equal to
>	Greater than
<	Less than
>=	Greater than or equal to
<=	Less than or equal to

The ' \leq ' operation is also used to signify 'taking on the value of'

Sequential Statements

A PROCESS is used to describe sequential events and is included in the ARCHITECTURE of the design.

An ARCHITECTURE can contain several PROCESS statements.

PROCESS statements have 3 parts:

Sensitivity list :

includes signals used in the PROCESS

process is activated when a signal in sensitivity list changes value

PROCESS :

the description of behavior

END statement:


describes the end of the PROCESS

Process - Sequential Statement

Simple example of PROCESS

```
mux: PROCESS (a, b, s) -- the sensitivity list
BEGIN
    IF ( s = '0' ) THEN
        x <= a;
    ELSE
        x <= b;
    END IF;
END PROCESS mux;
```

-- define the process section

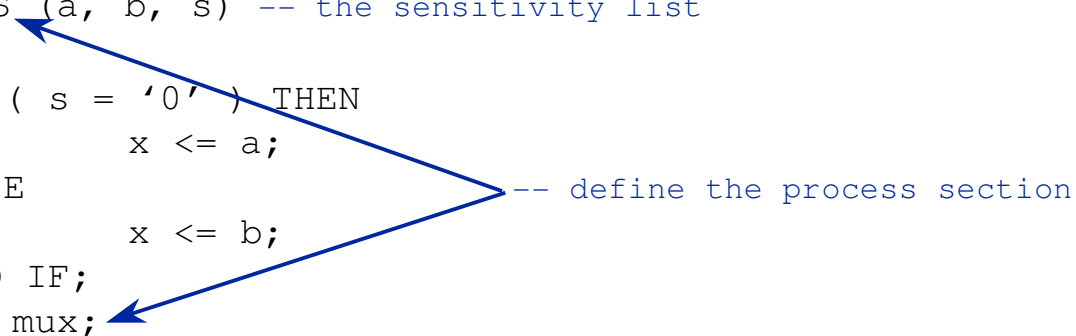

Here the process 'mux' is sensitive to signals 'a', 'b' and 's'. Whenever signal 'a' or 'b' or 's' changes value, the statements inside the process will be evaluated

IF - THEN - ELSE

IF is a sequential statement and can only be used in PROCESS
To select a specific execution path based on Boolean evaluation of a condition
or set of conditions

```
PROCESS (sel, a, b, c, d)
BEGIN
    IF (sel = "00") THEN
        step <= a;
    ELSIF (sel = "01") THEN
        step <= b;
    ELSIF (sel = "10") THEN
        step <= c;
    ELSE
        step <= d;
    END IF;
END PROCESS;
```

Must have an “END IF” statement for every “IF” statement

Caution using “IF-THEN-ELSE”



The following PROCESS does not specify the value of “q” when “a1” is equal to “0”, thus creating a “Latch”.

```
PROCESS (a1, d)
BEGIN
    IF (a1 = '1') THEN
        q <= d;
    END if;
END PROCESS;
```

The following PROCESS specifies the value of “q” when “a1” is equal to “0”, thus creating an AND gate.

```
PROCESS (a1, d)
BEGIN
    IF (a1 = '1') THEN
        q <= d;
    ELSE null; -- don't care
    END if;
END PROCESS;
```

CASE - WHEN

CASE is a sequential statement and can only be used in PROCESS

```
ARCHITECTURE archdesign OF design IS
BEGIN
    decode: PROCESS (a, b, c, option)
    BEGIN
        CASE option IS
            WHEN "00"    => output <= a;
            WHEN "01"    => output <= b;
            WHEN "10"    => output <= c;
            WHEN OTHERS => output <= '0';
        END CASE;
    END PROCESS decode;
END archdesign;
```

OTHERS is all other possible value for signals of type std_logic

Caution using “CASE-WHEN”



This PROCESS generates an unwanted latch because not all states are defined.

```
PROCESS (set, a, b)
BEGIN
  CASE sel IS
    WHEN "00" => q<=a;
    WHEN "11" => q<=b;
  END CASE;
END PROCESS;
```

This PROCESS generates a multiplexer correctly because states “10” and “01” are defined.

```
PROCESS (set, a, b)
BEGIN
  CASE sel IS
    WHEN "00"    => q<=a;
    WHEN "11"    => q<=b;
    WHEN OTHERS => q<='0';
  END CASE;
END PROCESS;
```

Data Objects

SIGNAL statement

used to declare internal signals; external signals are declared in port statement of entity

interconnects components or processes

may be assigned to an external signal

```
ARCHITECTURE behavior OF example IS
    SIGNAL count:    std_logic_vector (3 downto 0);
    SIGNAL flag:     std_logic;
    SIGNAL mtag:     std_logic_vector (0 to 3);
    SIGNAL stag:     std_logic_vector (6 downto 0);
BEGIN
-- always declared in ARCHITECTURE section
```

represents state elements in a state-machine

```
ARCHITECTURE behavior OF example IS
    TYPE states IS (state0, state1, state2, state3);
    SIGNAL memread:  states;
BEGIN
-- each state (state0, state1, etc.) represents a distinct state.
```

Data Objects

CONSTANT

holds a specific value of a type that cannot be changed within the design description

```
ARCHITECTURE behavior OF example IS
    CONSTANT width: integer := 8;
BEGIN
    -- "width" is a constant with integer type and has a value of
    "8"
```

VARIABLE

used to declare local values only within a given PROCESS.

```
PROCESS (s)
    VARIABLE count: std_logic;
BEGIN
    -- value of "count" may be modified within this PROCESS
```

REGISTERS in Behavioral VHDL

3 ways to describe a register

```
PROCESS (clk)
    BEGIN
        IF (clk'event AND clk='1') THEN    -- rising edge of clk
            q <= d;
        END IF;
    END PROCESS;
-- falling edge of clk => (clk'event AND clk = '0')
```

```
PROCESS (clk)
    BEGIN
        IF RISING_EDGE (clk) THEN
            q <= d;
        END IF;
    END PROCESS;
```

```
PROCESS                                     -- no sensitivity list
    BEGIN
        WAIT UNTIL clk'event AND clk = '1';
            q <= d;
    END PROCESS;
```

Synchronous Reset

```
upcount: PROCESS (clock)
  BEGIN
    IF (clock'EVENT AND clock = '1') THEN
      IF reset = '1' THEN
        count <= 0; -- synchronous
      ELSE
        count <= count + 1;
      END IF;
    END IF;
  END PROCESS upcount;
```

Only **CLOCK** is in the sensitivity list because the process becomes activated only during clock transition

Asynchronous Reset

```
upcount: PROCESS (clock, reset)
  BEGIN
    IF (reset = '1') THEN      -- reset has higher priority
      count <= 0;             -- asynchronous
    ELSIF (clock'EVENT AND clock = '1') THEN
      count <= count + 1;
    END IF;
  END PROCESS upcount;
```

This process is sensitive to changes in both CLOCK and RESET, therefore both signals are included in the sensitivity list

LATCHES - in Behavioral VHDL

example of a D-Latch

```
ARCHITECTURE behavior OF dlatch IS
BEGIN
    PROCESS (ina, enable)
    BEGIN
        IF (enable = '1') THEN
            outa <= ina;
        END IF;
    END PROCESS;
END behavior;
```

example of an SR-Latch

```
ARCHITECTURE behavior OF srlatch IS
BEGIN
    PROCESS (set, reset)
    BEGIN
        IF (set = '1' AND reset = '0') THEN
            outa <= '1';
        ELSIF (set = '0' AND reset = '1') THEN
            outa <= '0';
        END IF;
    END PROCESS;
END behavior;
```

Hierarchical Designs



Advantages:

Allows duplication of common building blocks

Components (VHDL models or schematic symbols) can be created, tested and held for reuse

Smaller components can be more easily integrated with other blocks

Design becomes more readable

Design becomes easier to debug

Design can be partitioned into groups and re-used by other design teams

VHDL testbenches can be used to generate stimuli

COMPONENT



Lower level design

```
ENTITY add IS
PORT(op1,op2 : IN  std_logic_vector(2 downto 0);
      result  : OUT std_logic_vector(3 downto 0) );
END add;

ARCHITECTURE dataflow OF add IS
BEGIN
result <= op1 + op2;
END dataflow;
```

Lower level design can be instantiated in a higher level entity that may be in a separate file or in the same file

Device under test can be instantiated in the higher level testbench

COMPONENT (cont'd)

COMPONENT statement is a declaration of an VHDL entity which can be instantiated (placed) within other models

Example

```

ENTITY addmult IS
PORT (sig1,sig2 : IN  std_logic_vector (2 downto 0);
      res       : OUT std_logic_vector (4 downto 0) );
END addmult;


ARCHITECTURE structure OF addmult IS
    SIGNAL s_add: std_logic_vector (3 downto 0);
    COMPONENT add  -- component declaration (like entity
                   declaration)
    port(op1,op2 : IN  std_logic_vector (2 downto 0);
         result  : OUT std_logic_vector (3 downto 0));
    END component;

BEGIN
    add1: add PORT MAP(op1=>sig1, op2=>sig2, result=>s_add);
    res <= s_add * 2;
END structure;

```

name of lower level entity

key word connecting two levels

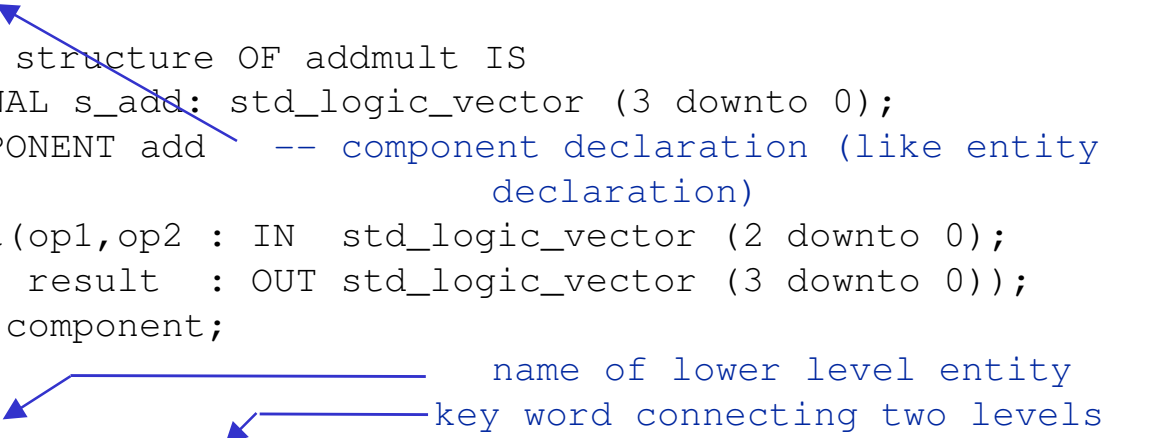

VHDL Testbenches

A testbench in VHDL provides the design under test with user defined input signals described in VHDL

A VHDL testbench is tool and architecture independent

The testbench consists of

- an empty entity

- an architecture describing the behavior of the testbench

- the design under test included as a component

- signals for the port connections

- a port map connecting the design under test

- processes and concurrent statements defining the waveforms of the test signal

The testbench is the top level of a hierarchical design

For/Use statements connect entities and components in hierarchical designs

Configurations allow different combinations of entities and architectures

Testbench Example

```
LIBRARY ieee;

ENTITY device IS
PORT (clk, rst, din : IN std_logic;
      dout          : OUT std_logic);
END device;

ARCHITECTURE device_arch OF device IS
BEGIN
    PROCESS(rst,clk)
    BEGIN
        ...
    END PROCESS;
END device_arch;
```

```
LIBRARY ieee;
ENTITY test_device IS
END test_device;
ARCHITECTURE test_device_arch OF test_device IS
    COMPONENT device
    PORT (clk, rst, din : IN std_logic;
          dout          : OUT std_logic);
    END component;
    SIGNAL clk_in,rst_in,din_in,dout_out : std_logic;
BEGIN
    dut:device PORT MAP(clk_in, rst_in, din, dout);
    clk_driver:process
    BEGIN
        clk <= '1';
        wait for 20 ns;
        clk <= '1';
        wait for 20 ns;
    END PROCESS;
    rst <= '0';
    din_in <= '1';
END device_arch;
```

Device under test

Testbench

CPLD Optimization - Output Enables


VHDL does not have an explicit OE, therefore need to describe the function of OE

```

ENTITY oe IS
    PORT (d      : IN  std_logic_vector (6 downto 0);
          q      : OUT std_logic_vector (6 downto 0);
          oe,clk : IN  std_logic );
END oe;

ARCHITECTURE behavioral OF oe IS
    SIGNAL qint : std_logic_vector (6 downto 0);
BEGIN
    dff: PROCESS (clk)
    BEGIN
        IF (clk' event and clk='1') THEN
            qint <= d;
        END IF;
    END PROCESS;
    q <= "ZZZZZZ" WHEN (oe ='0')
        ELSE qint;
END behavioral;

```

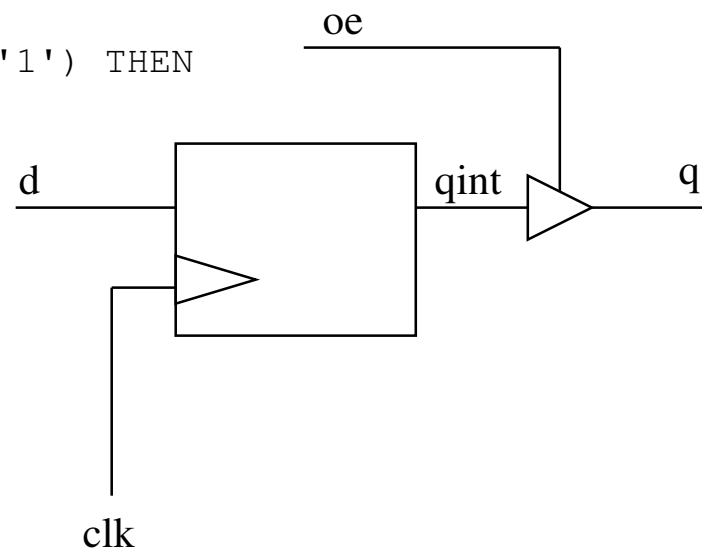


CPLD Optimization - BiDirectional Signals

```
--      "data" is bi-directional EXTERNAL signal
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;


ENTITY loadctr IS
    PORT (clock, load, oe : IN    std_logic;
          data           : INOUT std_logic_vector(7 DOWNTO 0) );
END loadctr;

ARCHITECTURE archloadctr OF loadctr IS
    SIGNAL count: std_logic_vector(7 DOWNTO 0);
BEGIN
    PROCESS (clock)
    BEGIN
        IF (clock'EVENT AND clock = '1') THEN
            IF load = '1' THEN
                count <= data;
            ELSE
                count <= count + 1;
            END IF;
        END IF;
        data <= "ZZZZZZZZ" WHEN oe = '0' ELSE count;
    END PROCESS;
END archloadctr;
```

 

Moore State Machine

Moore State Machine


 


CPLD Optimization

State Machine Moore



Bringing the Best Together

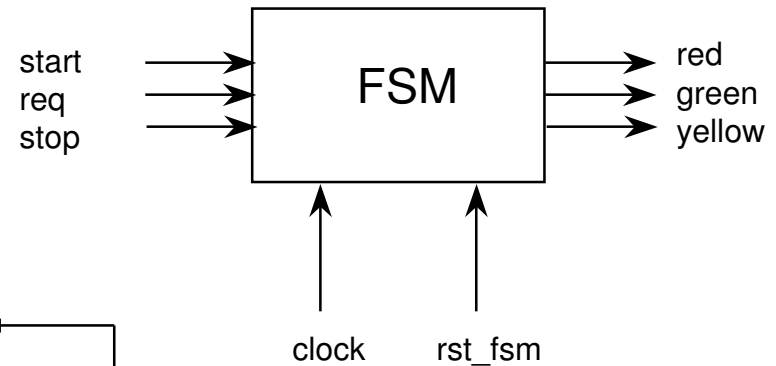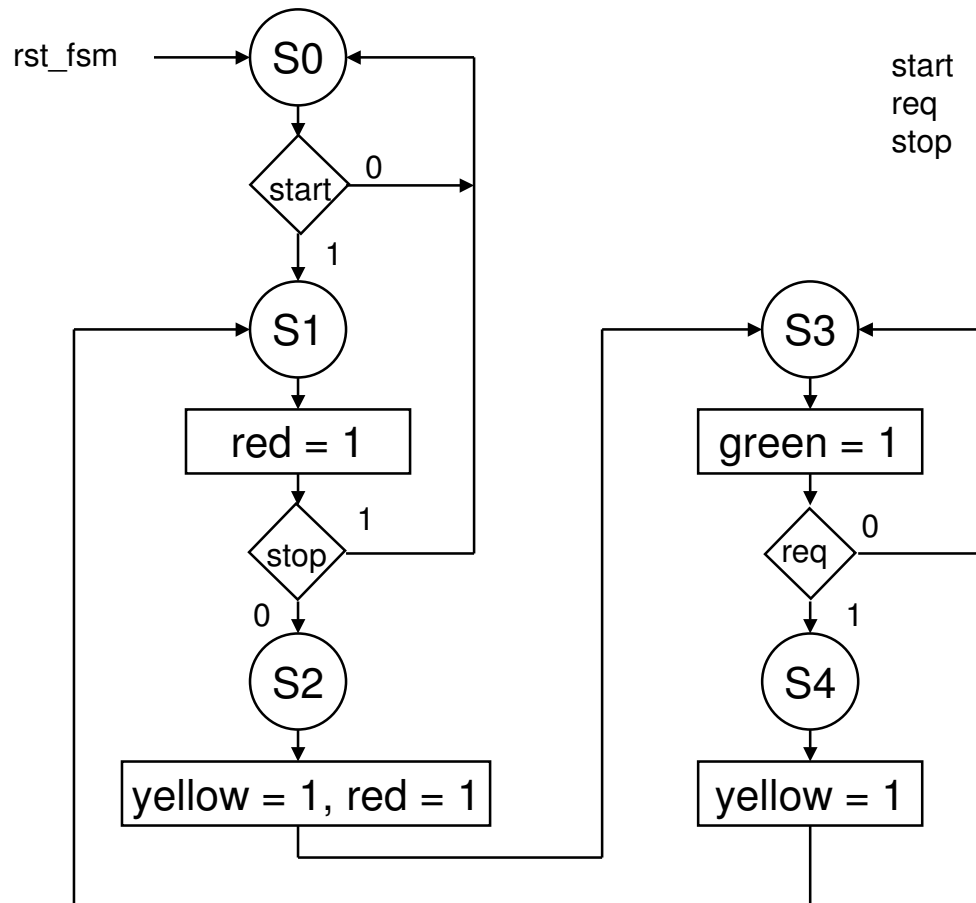

CPLD Optimization State Machine Moore



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY traffic_light IS
    PORT(clock, rst_fsm      : IN  std_logic;
         start, req, stop    : IN  std_logic;
         red, green, yellow : OUT std_logic );
END;

ARCHITECTURE fsm_moore OF traffic_light IS

TYPE states IS (S0, S1, S2, S3, S4);
SIGNAL value, nextvalue : states;

BEGIN

    reg: PROCESS (clock, rst_fsm)
    BEGIN
        IF (rst_fsm='1') THEN
            value <= S0;
        ELSIF (clock'EVENT AND clock='1') THEN
            value <= nextvalue;
        END IF;
    END PROCESS reg;
```

CPLD Optimization State Machine Moore

```
komb1: PROCESS (start, req, stop, value)
BEGIN
    CASE value IS
        WHEN S0 =>
            IF (start='1') THEN
                nextvalue <= S1;
            ELSE
                nextvalue <= S0;
            END IF;
        WHEN S1 =>
            IF (stop='1') THEN
                nextvalue <= S0;
            ELSE
                nextvalue <= S2;
            END IF;
        WHEN S2 =>
            nextvalue <= S3;
        WHEN S3 =>
            IF (req='1') THEN
                nextvalue <= S4;
            ELSE
                nextvalue <= S3;
            END IF;
        WHEN S4 =>
            nextvalue <= S1;
        WHEN OTHERS =>
            nextvalue <= S0;
    END CASE;
END PROCESS komb1;
```



Bringing the Best Together

CPLD Optimization State Machine Moore




```
komb2: PROCESS (value)
BEGIN
    red <= '0'; yellow <= '0'; green <= '0';
    CASE value IS
        WHEN S1 =>
            red <= '1';
        WHEN S2 =>
            yellow <= '1';
            red <= '1';
        WHEN S3 =>
            green <= '1';
        WHEN S4 =>
            yellow <= '1';
        WHEN OTHERS =>
            red <= '0';
            yellow <= '0';
            green <= '0';
    END CASE;
END PROCESS komb2;

END fsm_moore;
```


Mealy State Machine

Mealy State Machine

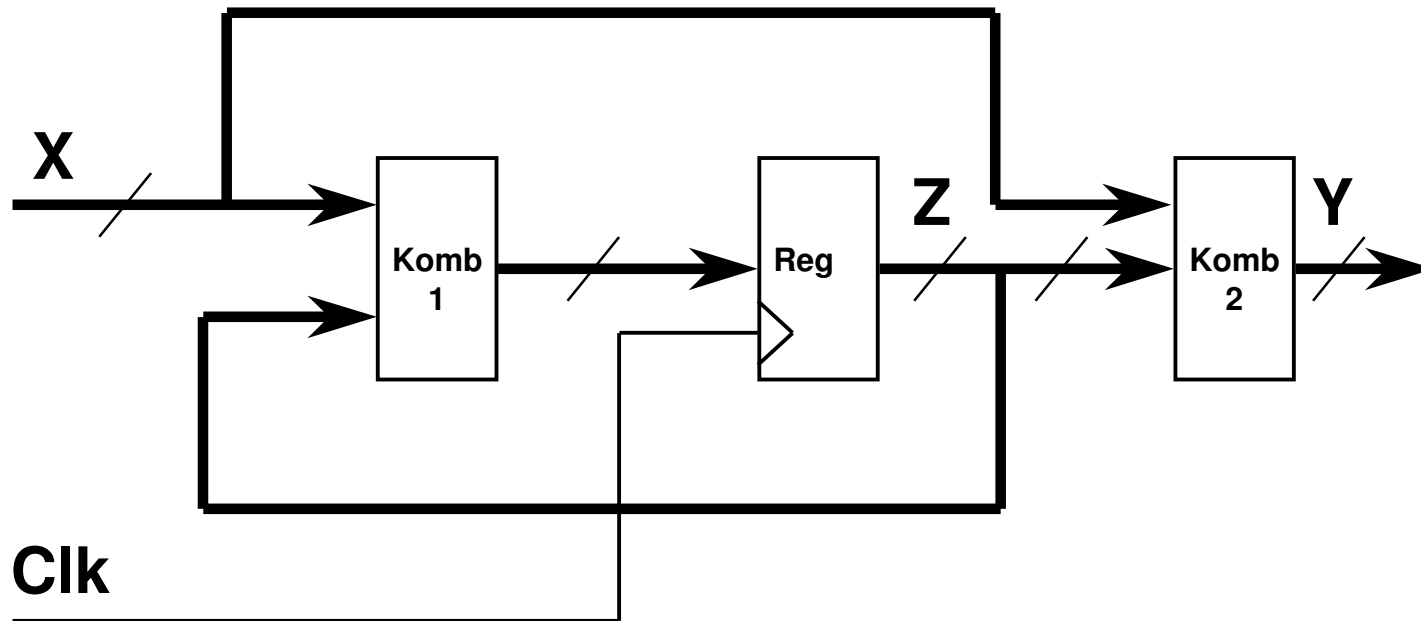

CPLD Optimization


State Machine Mealy

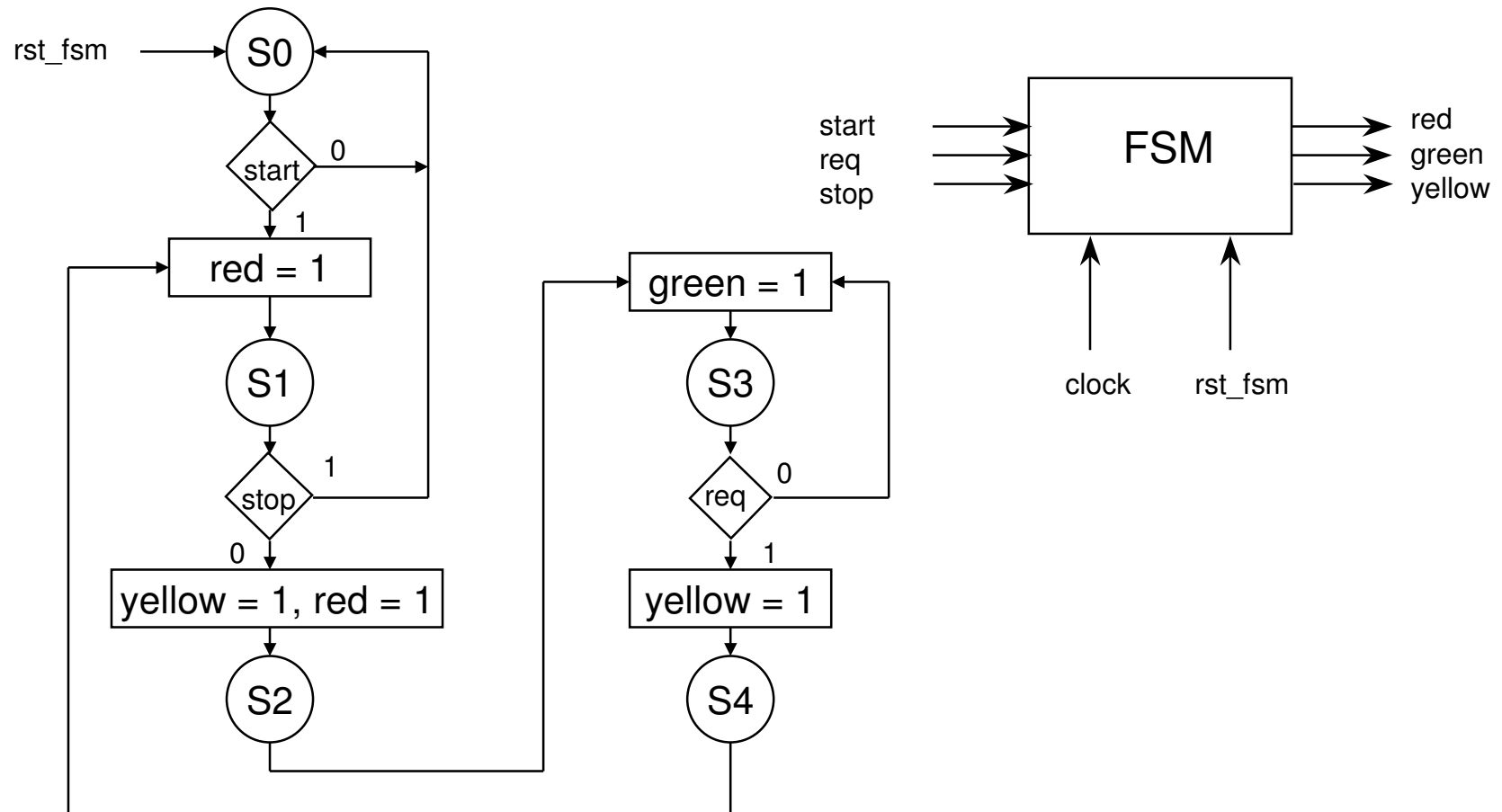

CPLD Optimization State Machine Medvedev



Medvedev State Machine

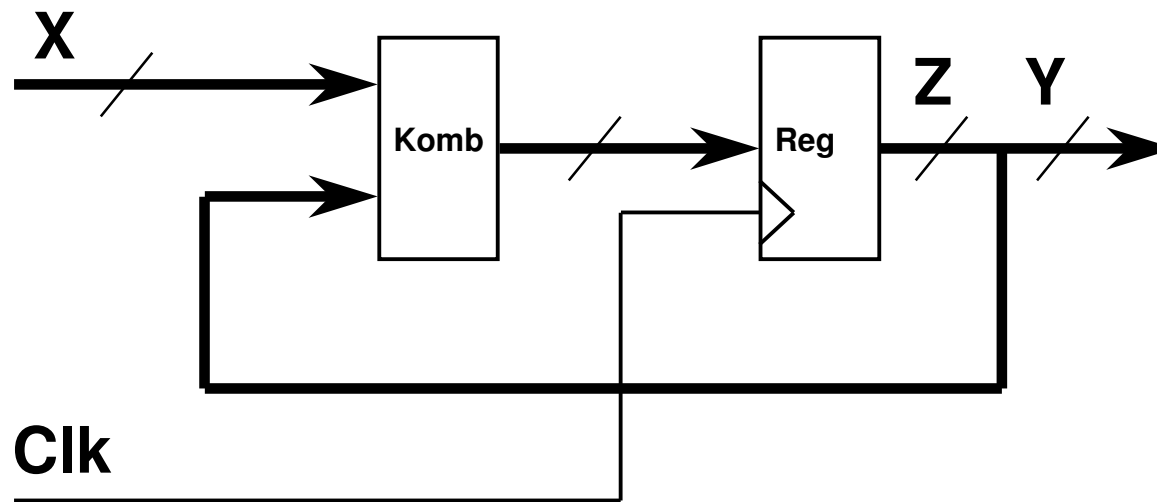

CPLD Optimization State Machine Medvedev



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY traffic_light IS
    PORT(clock, rst_fsm      : IN  std_logic;
         start, req, stop   : IN  std_logic;
         red, green, yellow : OUT std_logic );
END;

ARCHITECTURE fsm_med OF traffic_light IS

    SIGNAL states : std_logic_vector(2 downto 0);
    -- Reihenfolge der Ausgangsregister: red, green, yellow
    CONSTANT S0 : std_logic_vector(2 downto 0) := "000";
    CONSTANT S1 : std_logic_vector(2 downto 0) := "100";
    CONSTANT S2 : std_logic_vector(2 downto 0) := "110";
    CONSTANT S3 : std_logic_vector(2 downto 0) := "001";
    CONSTANT S4 : std_logic_vector(2 downto 0) := "010";

BEGIN
    komb_reg: PROCESS (clock, rst_fsm)
    BEGIN
        IF (rst_fsm='1') THEN
            states <= S0;
        ELSIF (clock'EVENT AND clock='1') THEN
            CASE states IS
                WHEN S0 =>
                    IF (start='1') THEN
                        states <= S1;
                    ELSE
                        states <= S0;
                    END IF;
            END CASE;
        END IF;
    END PROCESS;
END;
```

CPLD Optimization State Machine Medvedev



Bringing the Best Together

```
        WHEN S1 =>
            IF (stop='1') THEN
                states <= S0;
            ELSE
                states <= S2;
            END IF;
        WHEN S2 =>
            states <= S3;
        WHEN S3 =>
            IF (req='1') THEN
                states <= S4;
            ELSE
                states <= S3;
            END IF;
        WHEN S4 =>
            states <= S1;
        WHEN OTHERS =>
            states <= S0;
    END CASE;
END IF;

END PROCESS komb_reg;

red    <= states(2);
yellow <= states(1);
green  <= states(0);

END fsm_med;
```

CPLD Optimization - State Encoding



Many CPLD VHDL implementations use “one-hot” encoding. “One-hot” uses a register for each device state (state-per-bit), with only one register active (or “hot”) at a time.

Use “maximal” encoding for CPLDs it is typically faster and results in better device utilization

Don’t leave optimization solely to your tools; understand your device-architecture characteristics and tailor your design accordingly

Some tools automatically select an optimum state machine in response to your circuit implementation, guidance, or both (for example, prioritizing performance to the compiler), whereas other tools always default to one method unless you override them

Synplify has a checkbox “Symbolic FSM Compiler” which leads to an automatic recognition and special optimization of your FSMs if checked

CPLD Optimization - Undefined States



When all values are not explicitly defined, synthesis results may be unexpected

Whether using IF-THEN-ELSE, CASE-WHEN, WITH-SELECT-WHEN or WHEN-ELSE statements, not defining all possible values or states can result in unwanted “Latches”

Appendix I - Lattice Specific - Global OE



To use the Global OE available in the CPLD, simply lock the OE signal to the Global OE pin in the Fitter.

If the OE controls several different outputs in the design, ensure that the polarity are the same and the polarity is the same as the Global OE in the CPLD.

```
q <= "ZZZZZZZ" when (oe='0') else qint;
```

Appendix I - Lattice Specific - Global Reset I



To use the Global Reset pin in the CPLD, ensure that ALL reset signals in the ENTITY have the same reset name

Keep in mind that ALL registers have implied resets that connect to the Global Reset pin. If you specify a reset signal in your design, then you need to specify a reset signal for EVERY register and latch used. Otherwise, the Fitter will assign it to a PT reset

In the Fitter, you must specify to “use Global Reset”

Appendix I - Lattice Specific - Global Reset II



The following PROCESS does not specify a reset signal. There is however an implied reset signal (Global Reset) connected to the register.

```
PROCESS (clk)
BEGIN
    IF (clk'event AND clk = '1') THEN
        q <= d;
    END IF;
END PROCESS;
```

The following PROCESS specifies a reset signal. There is also an implied reset signal (Global Reset) connected to it. To make “rst” connect to Global Reset pin, must “use Global Reset” in the Fitter.

```
PROCESS (rst, clk)
BEGIN
    IF (rst = '1') THEN
        q <= '0';
    ELSIF (clk'event and clk = '1') THEN
        q <= d;
    END IF;
END PROCESS;
```


Appendix I - Lattice Specific - IO as a Register



VHDL file is similar to any Register description

```
ARCHITECTURE behavior OF ioreg IS
```

```
BEGIN
```

```
    PROCESS (rset, clka)
    BEGIN
```

```
        IF (rset = '1') THEN
            qout <= '0';
```

```
        ELSIF (clka'event AND clka = '1') THEN
            qout <= qin;
```

```
        END IF;
```

```
    END PROCESS;
```

```
END BEHAVIOR;
```

Appendix I - Lattice Specific - IO Cell as a Latch



VHDL file is similar to any D-type Latch description

```
ARCHITECTURE behavior OF iolatch IS
BEGIN
    PROCESS (le, qin)
    BEGIN
        IF (le = '1') THEN
            qout <= qin;
        END IF;
    END PROCESS;
END BEHAVIOR;
```

Literature



IEEE Standard VHDL Language Reference Manual

IEEE-1076-1992/B

Structured Logic Design with VHDL

J.R. Armstrong, F.G. Gray; Prentice Hall, Englewood Cliffs, 1993

Schaltungsdesign mit VHDL

Lehmann, Wunder; Franzis, ISBN 3-7723-6163-3

The VHDL Cookbook

P.J. Ashenden; via FTP *chook.adelaide.edu.au* or *du9ds4.fb9dv.uni-
duisburg.de*

A VHDL Primer

J. Bhasker, Prentice Hall 1992, ISBN 0-13-952987-X